

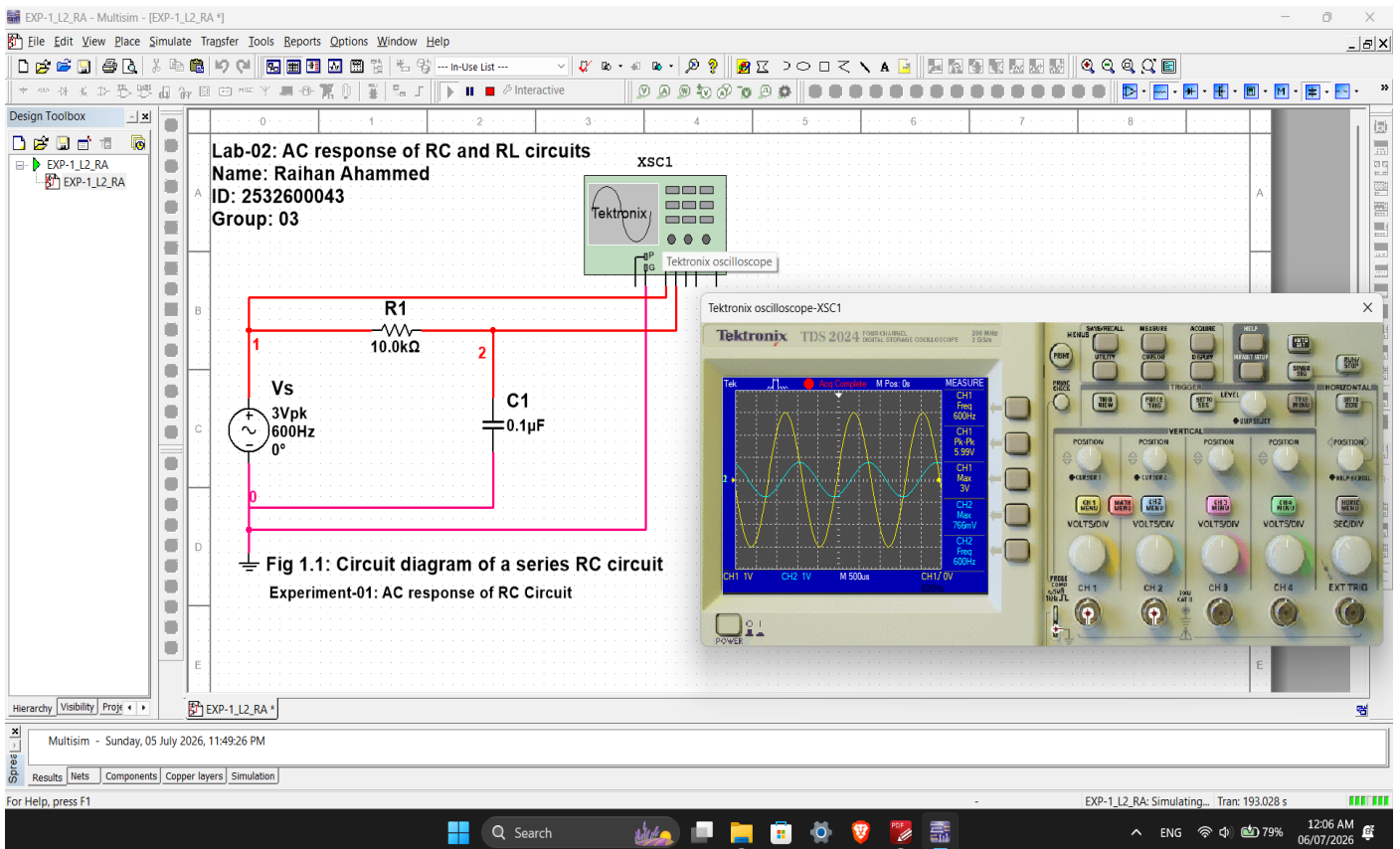
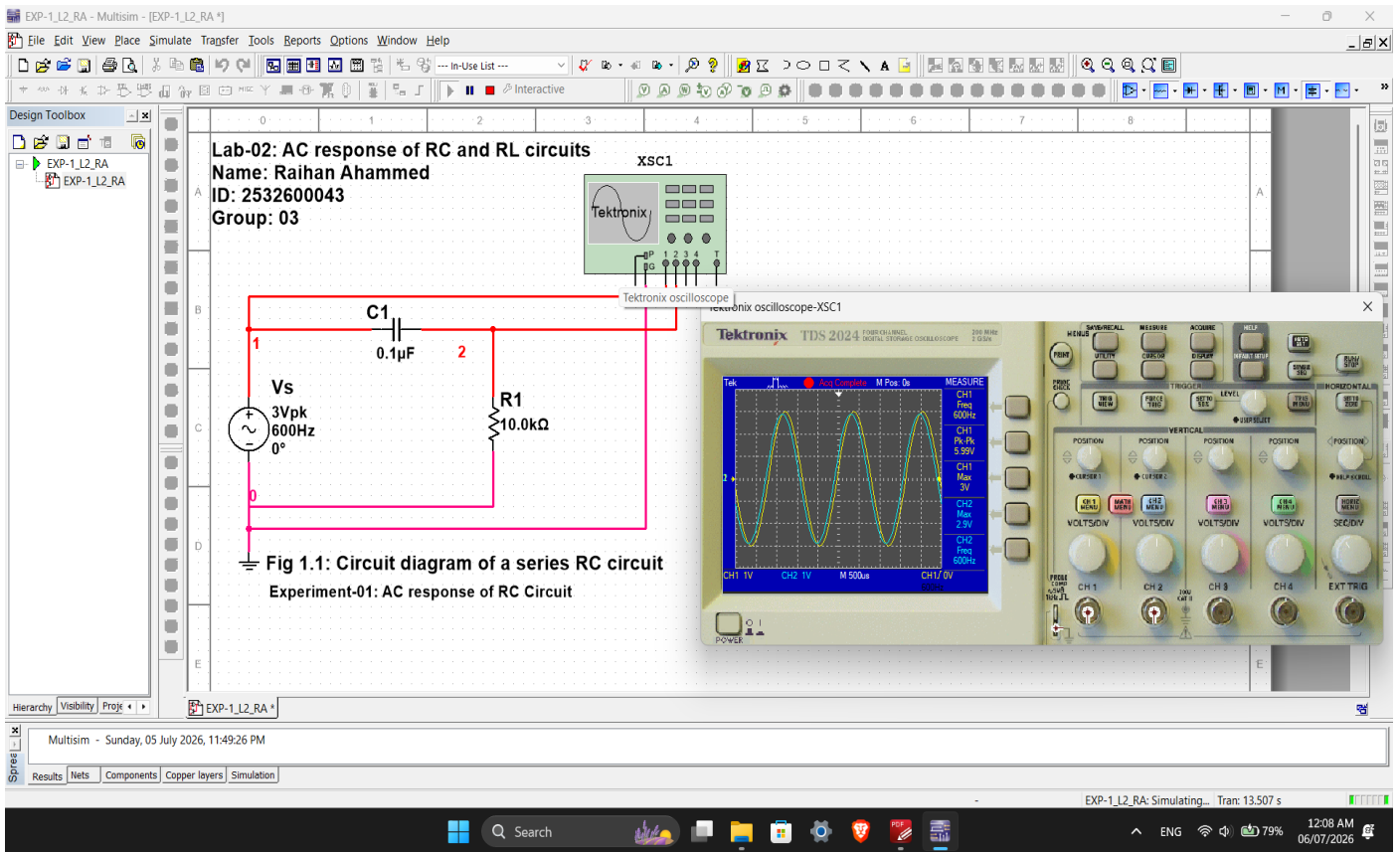


Lab-02: AC response of RC and RL circuits


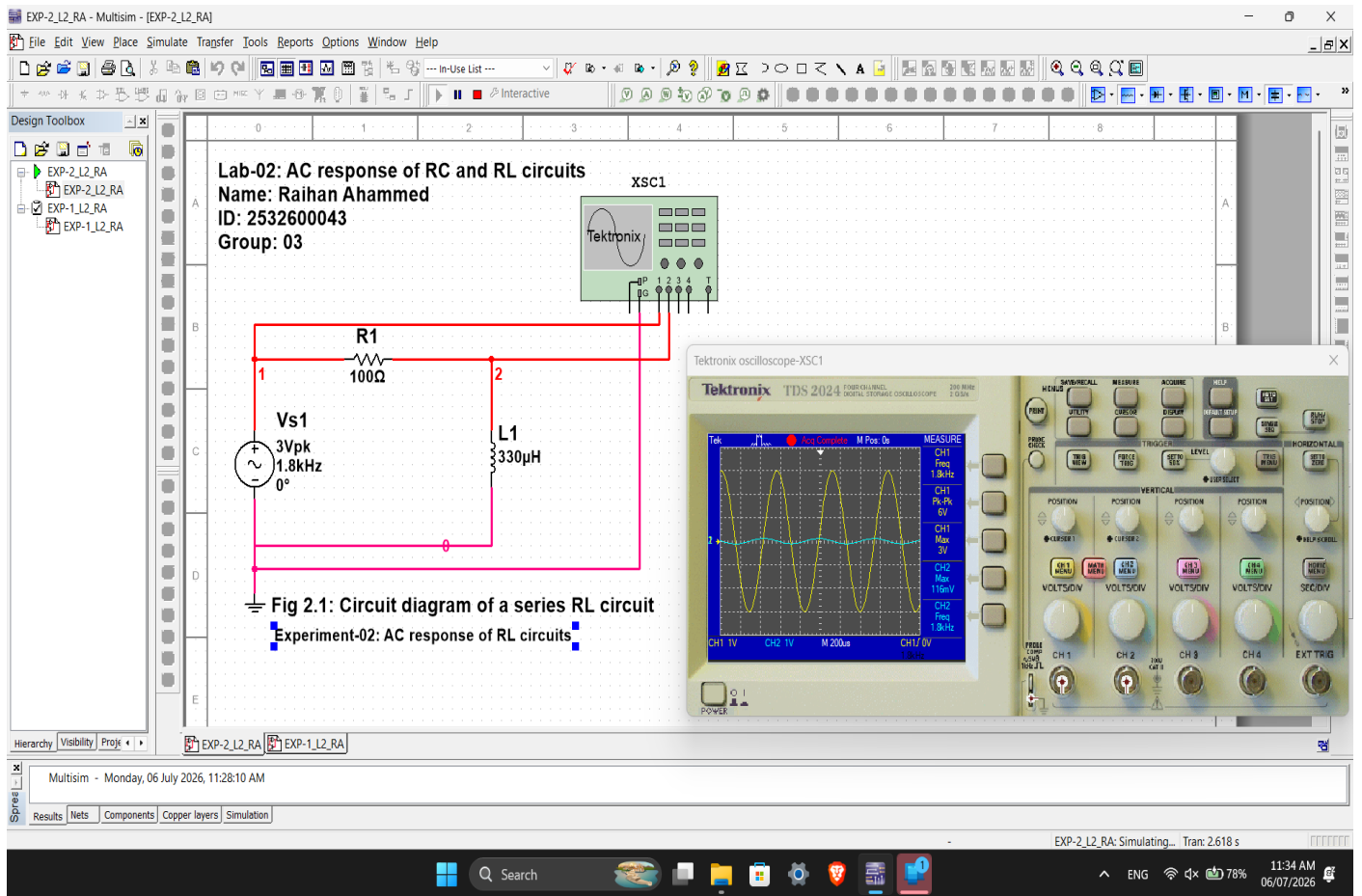
Name: Raihan Ahammed ID: 2532600043 Group: 03





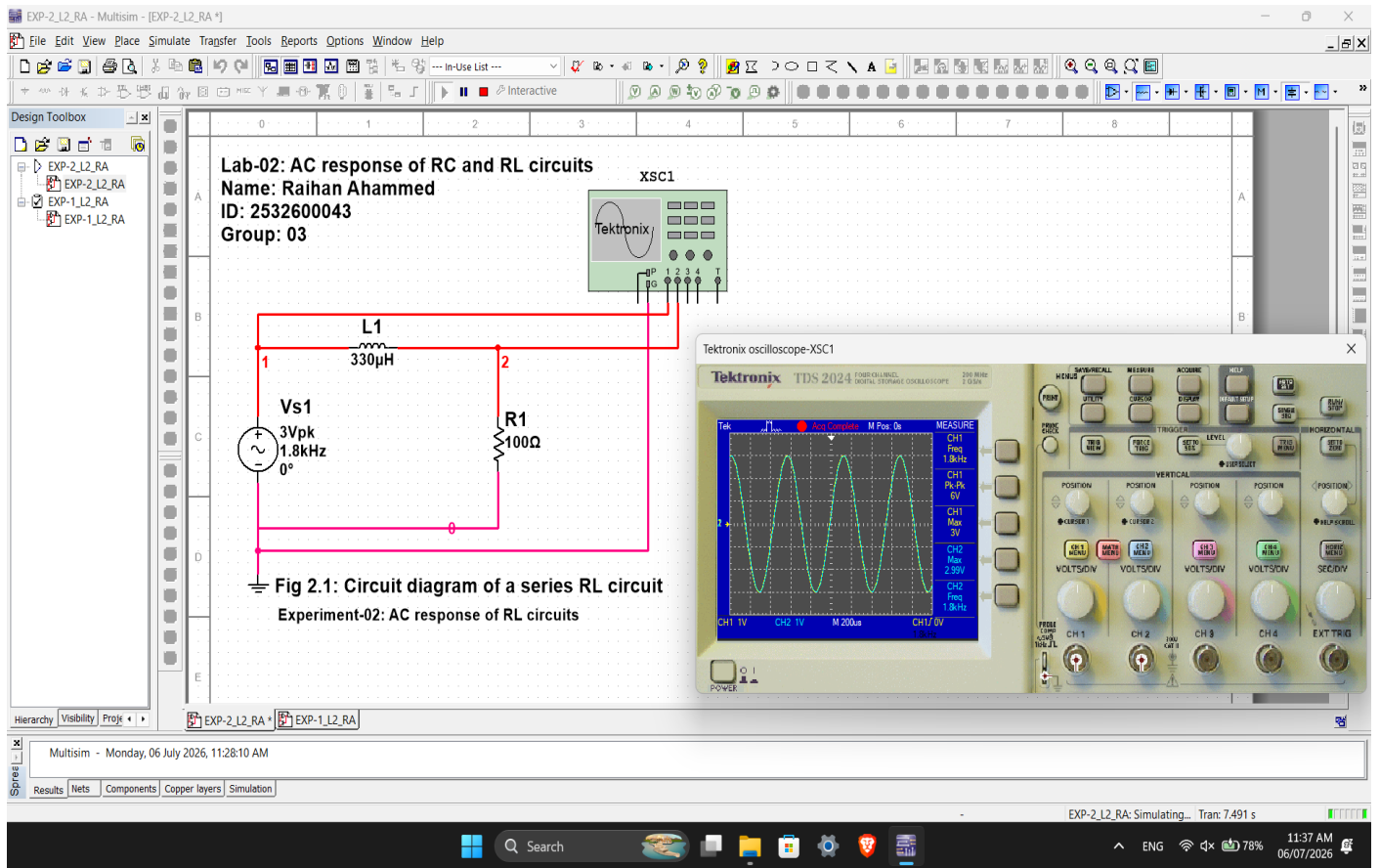



Lab-01: Verification of KVL and KCL

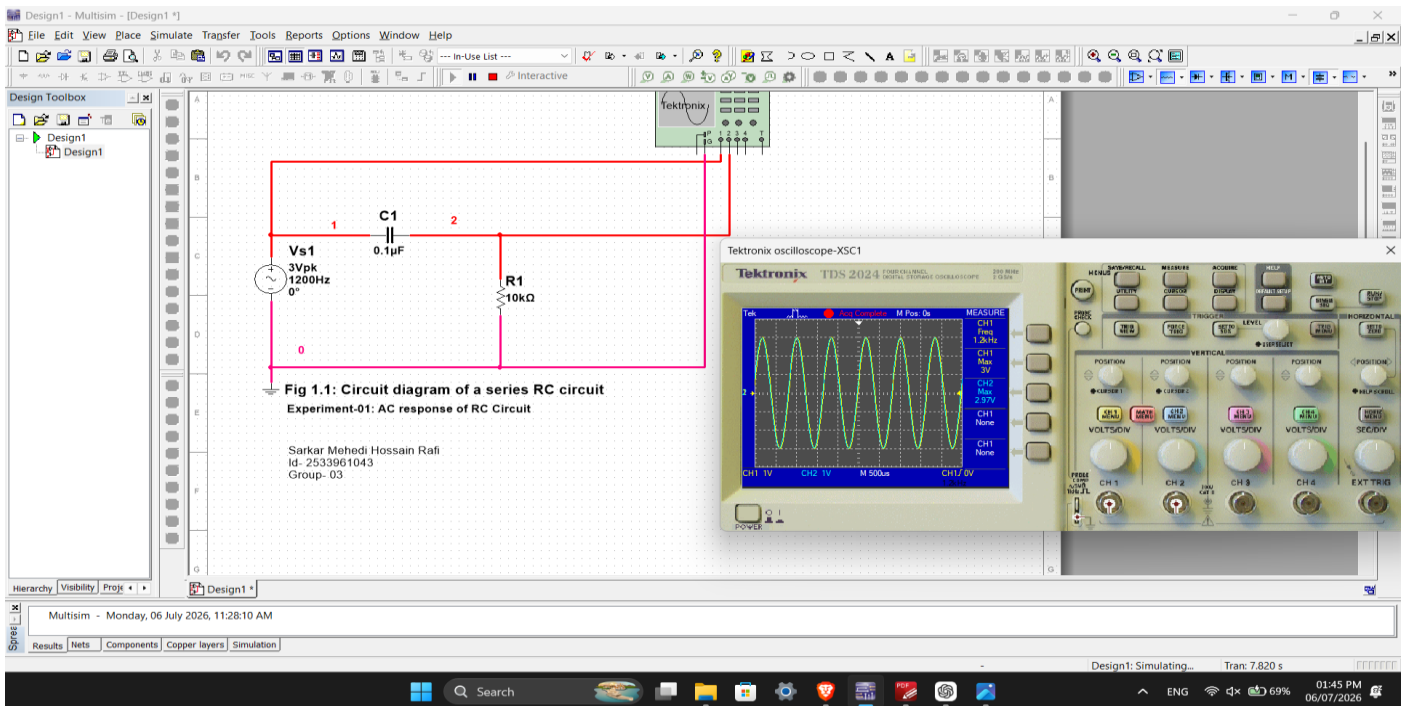
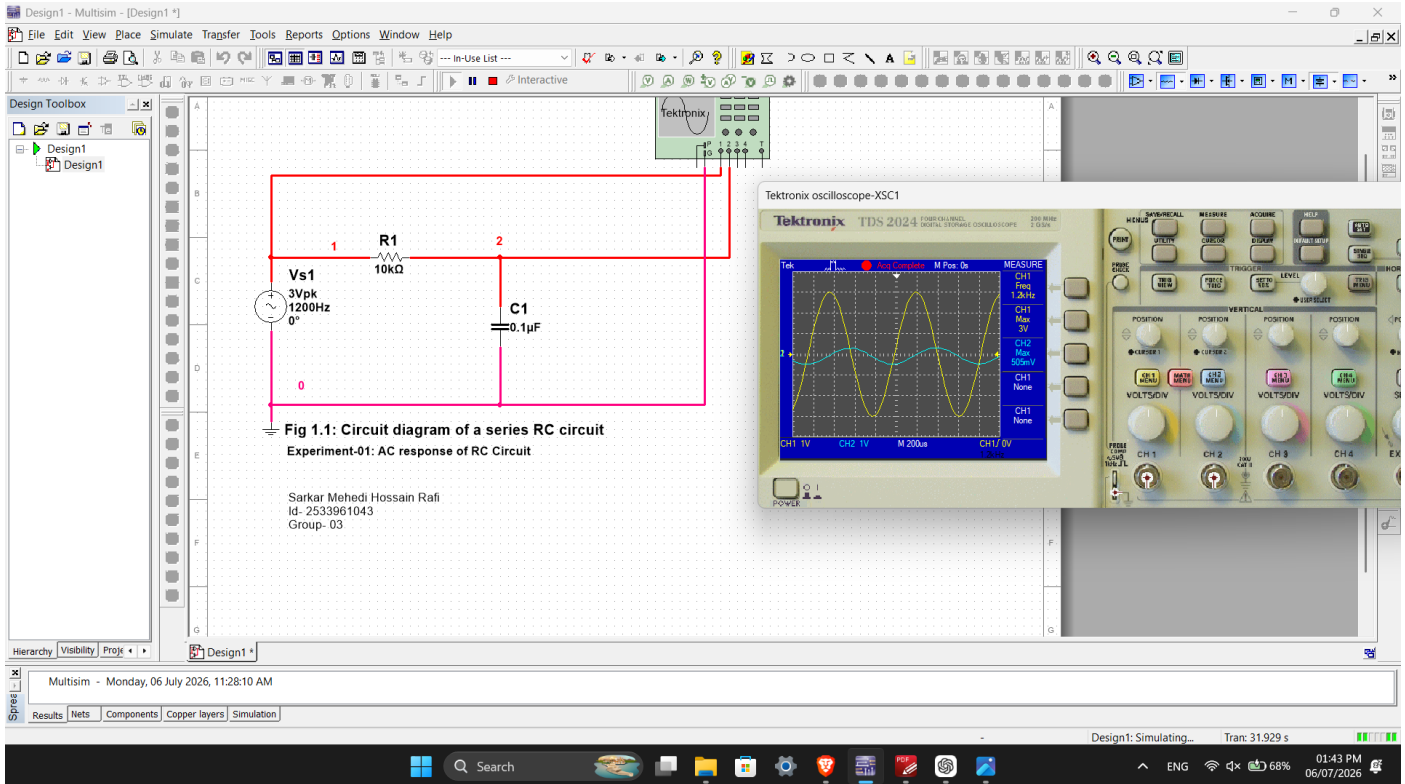
Name: Sarkar Mehedi Hossain Rafi ID: 2533961043 Group: 03



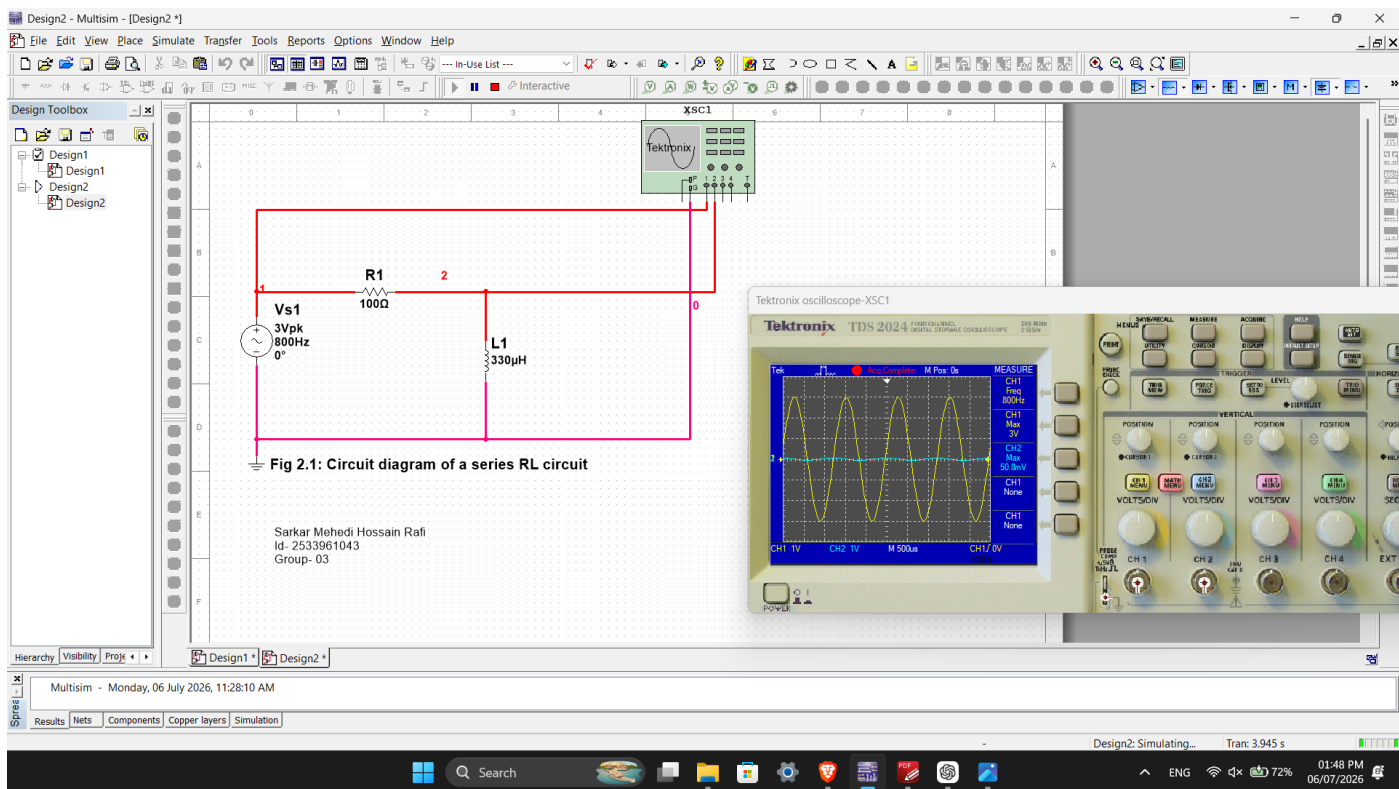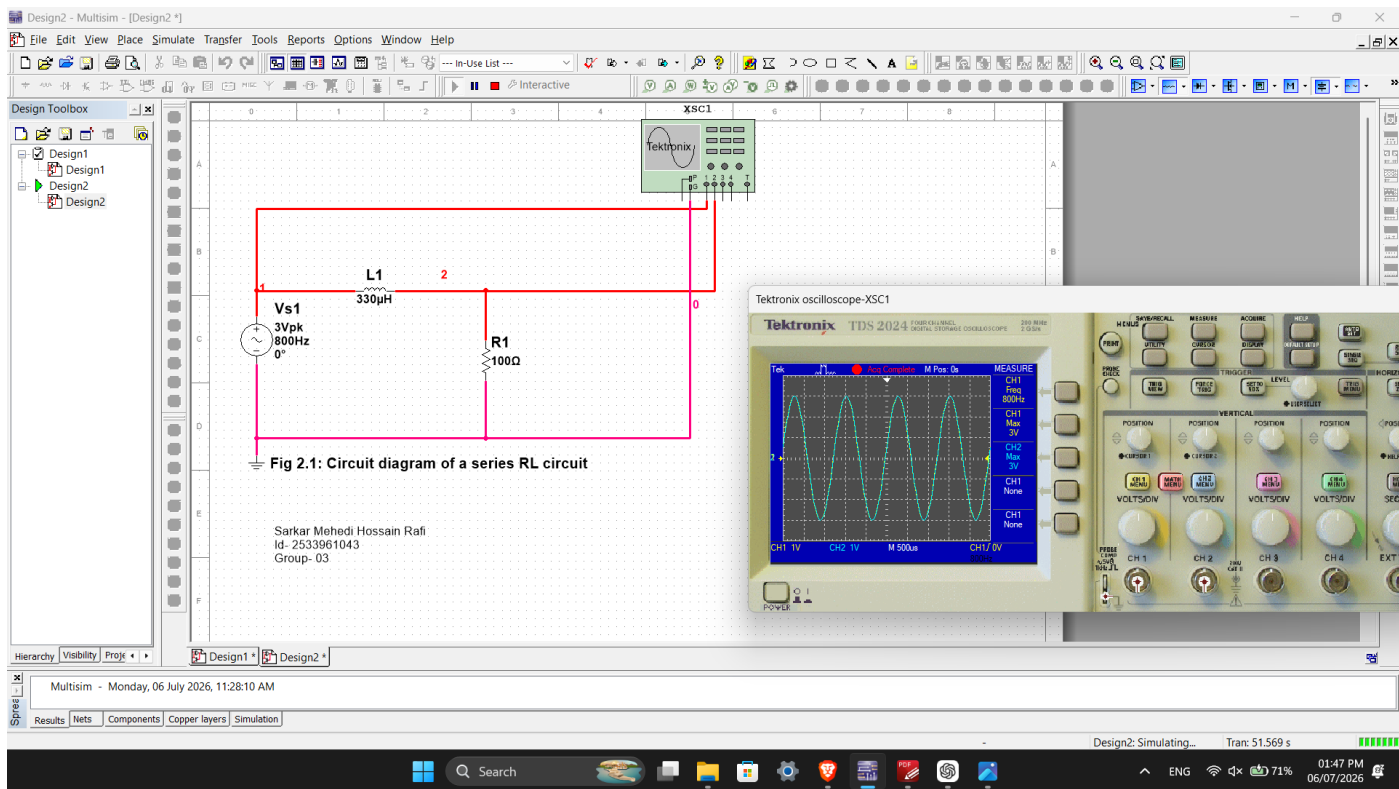


Name: ID: 2533961043 Group: 03

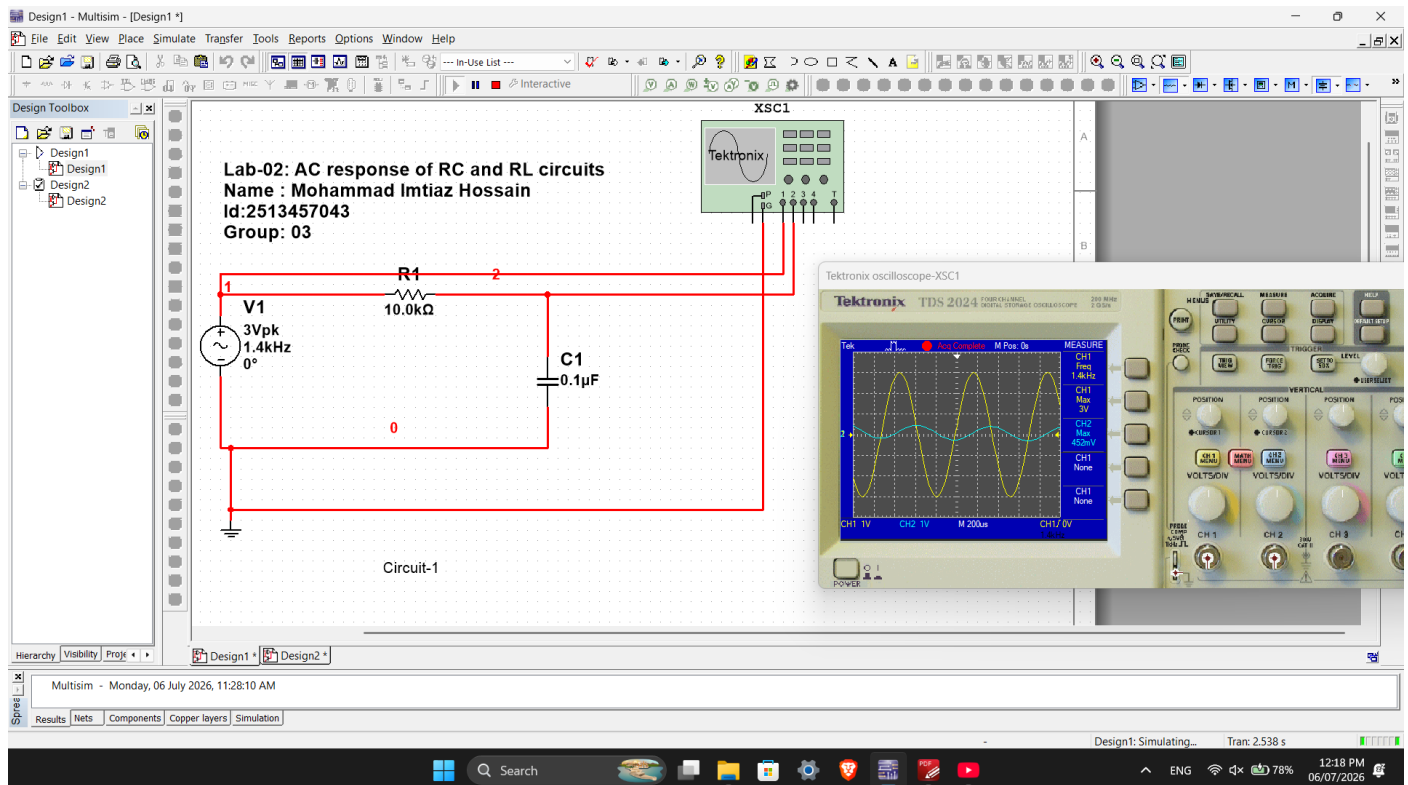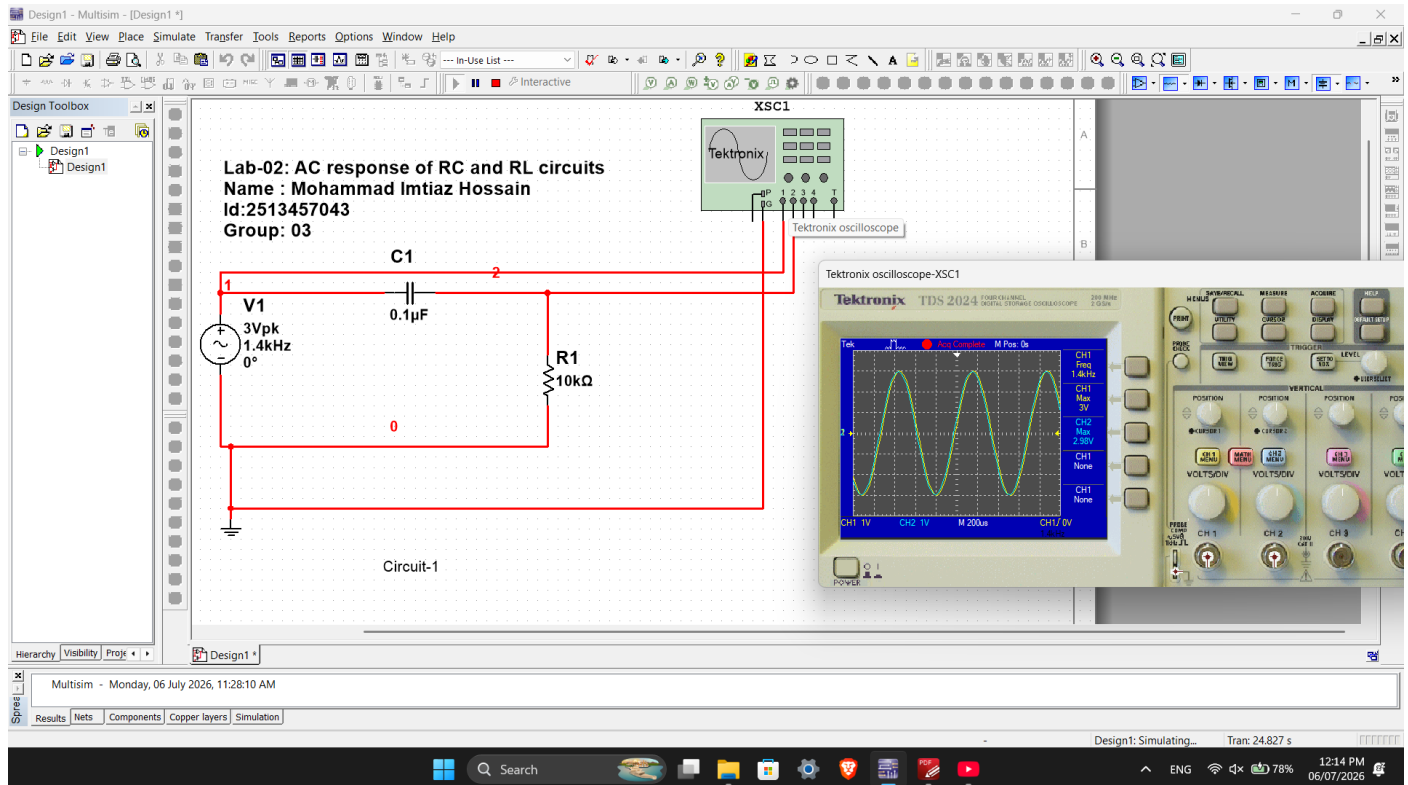


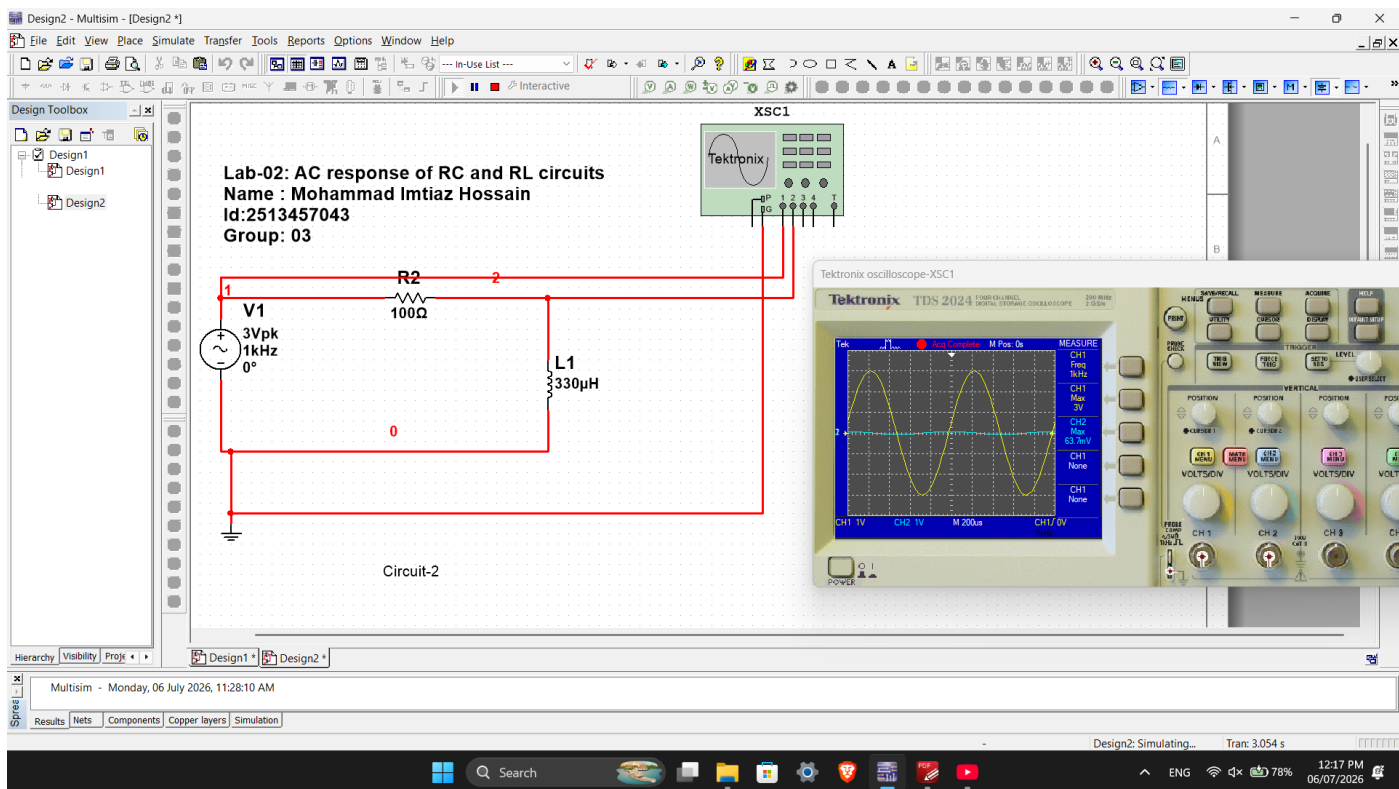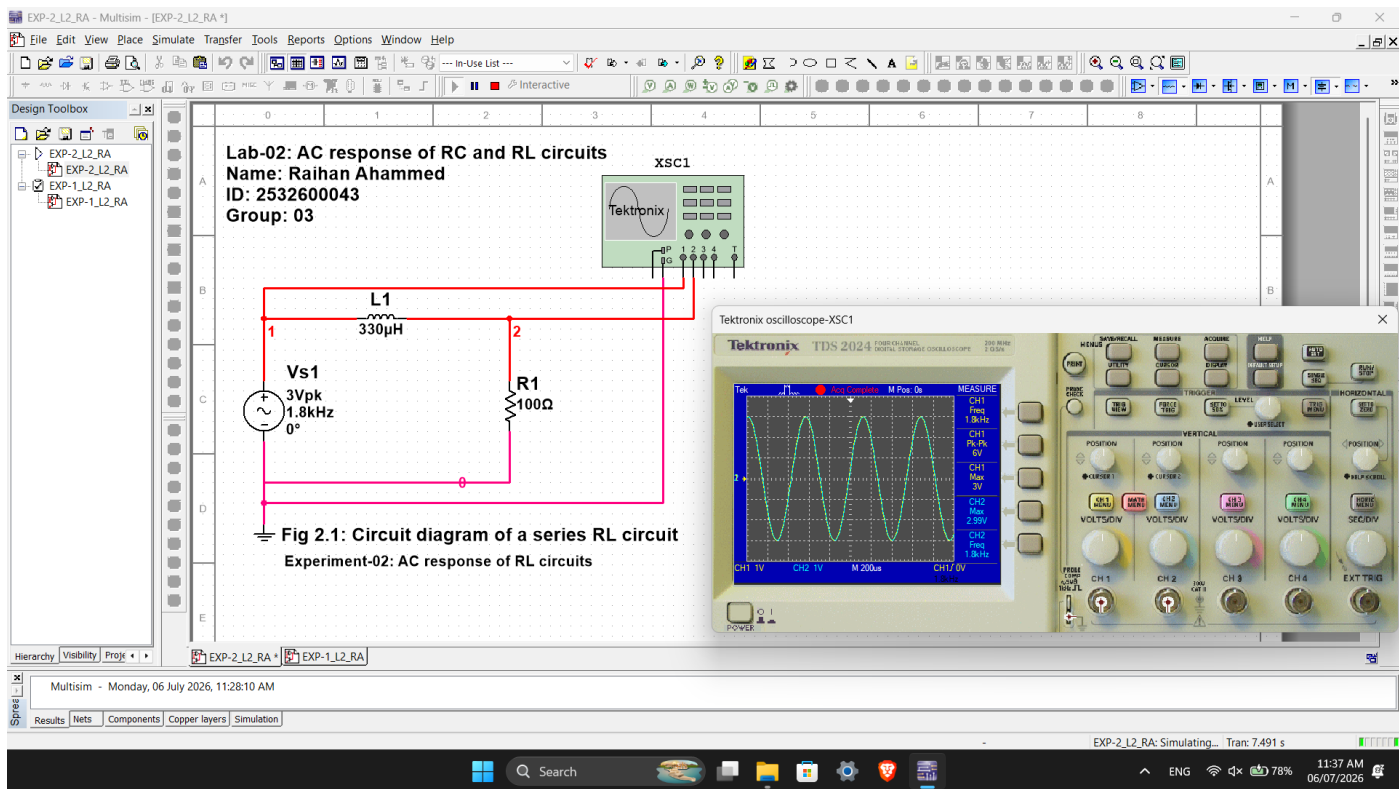


1. AC Response of C=0.1uF

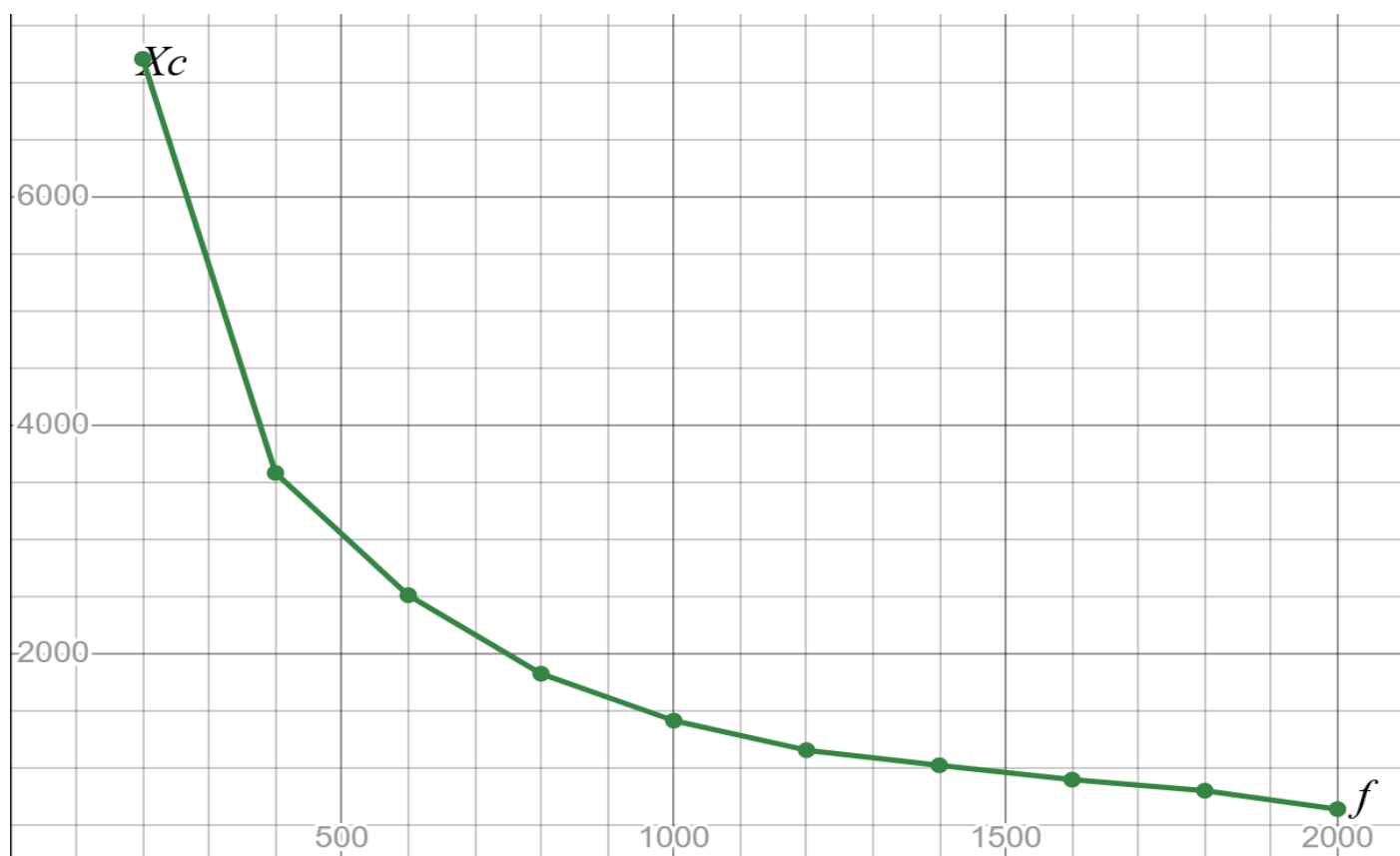

2. AC Response of C=0.4uF

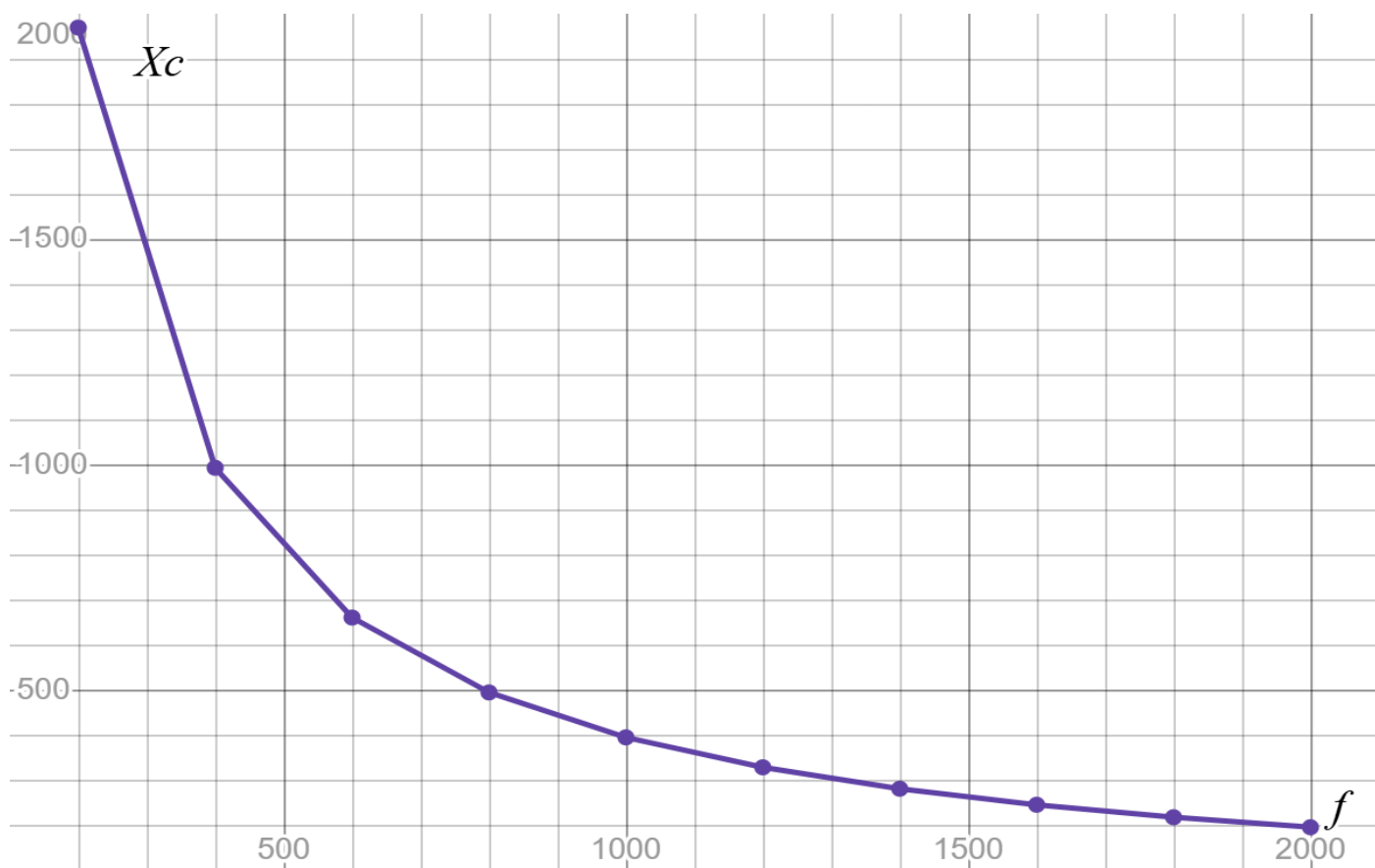

1. AC Response of L=330uH

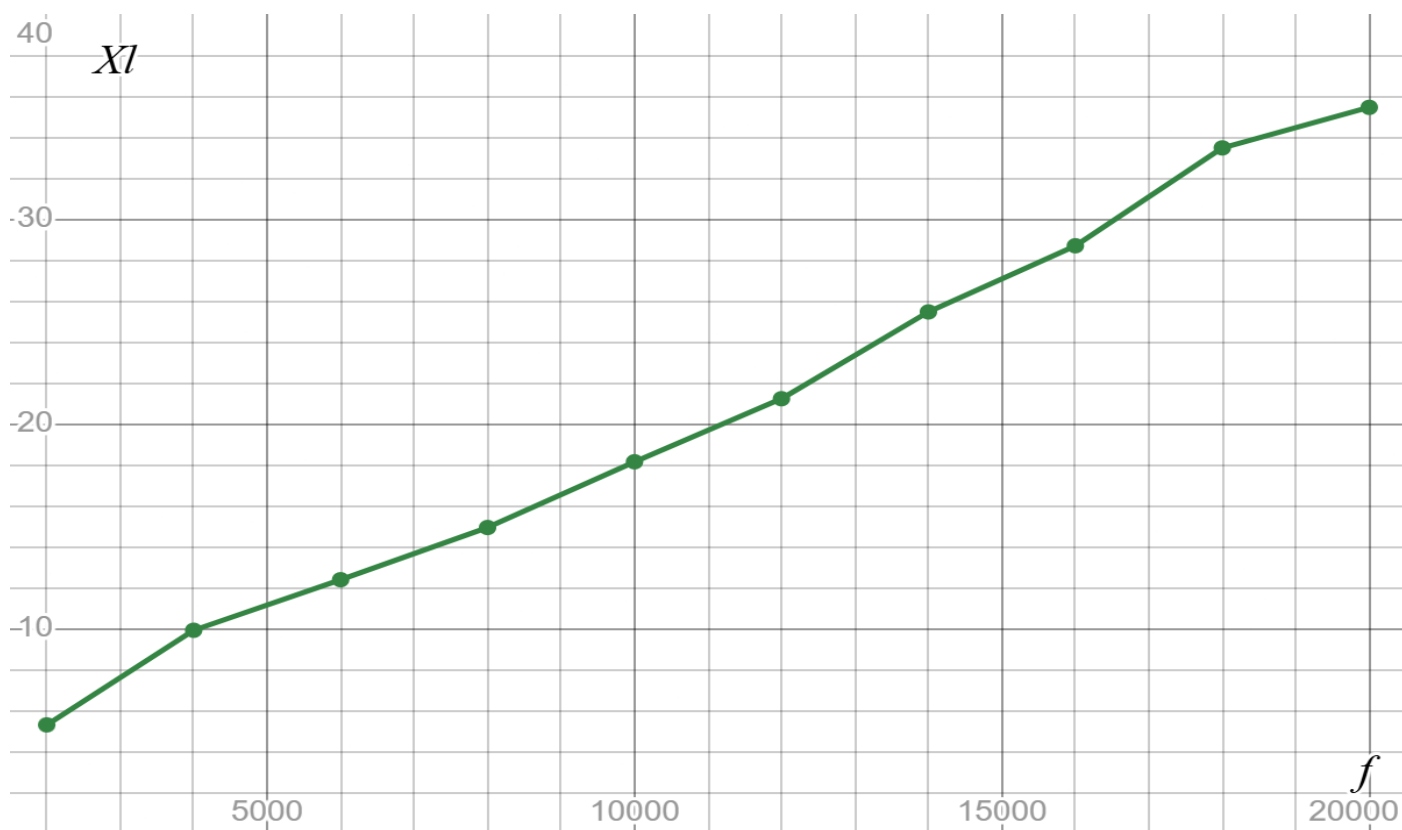

2. AC Response of L=600uH

