



North South University
Department of Electrical & Computer Engineering

LAB REPORT

Course Code: EEE241L

Course Title: Electrical Circuits II Lab

Semester: Summer '26

Course Instructor: Mr. Abu Obaidah (AbO) (Senior Lecturer)

Experiment Name:

AC response of RC and RL circuits

Experiment Number: 02

Experiment Date: 29-06-26

Section: 03

Date of Submission: 06-07-26

Group Number: 03

Submitted To: Lab Instructor: Sk Raziul Ahasan



Submitted By:



Score

Serial No	Student Name	ID	
1	Arafat Hossain Nirjon	2011871043	
7	Mohammad Imtiaz Hossain	2513457043	
26	Raihan Ahammed	2532600043	
34	Sarkar Mehedi Hossain Rafi	2533961043	

Lab-02: AC response of RC and RL circuits

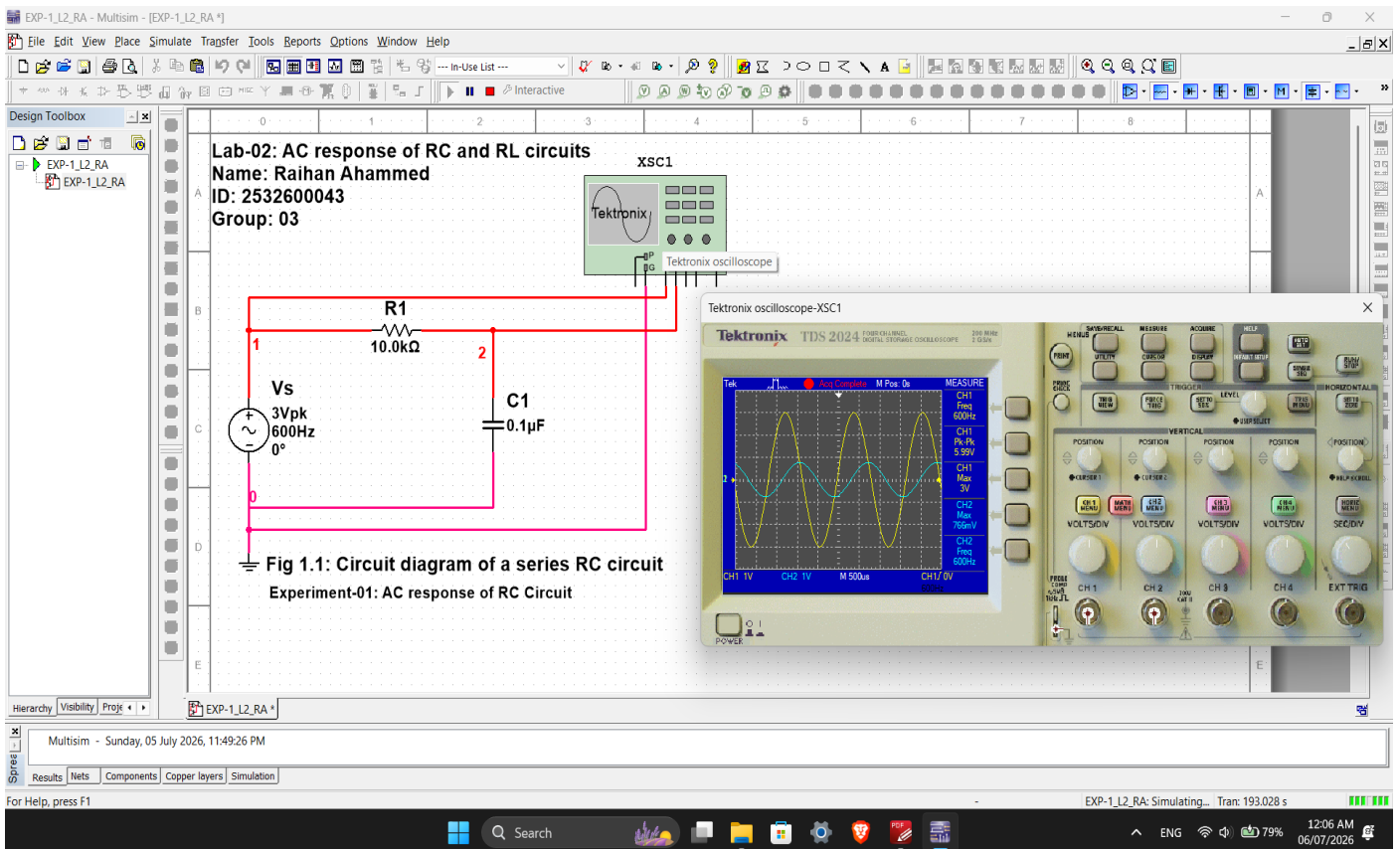
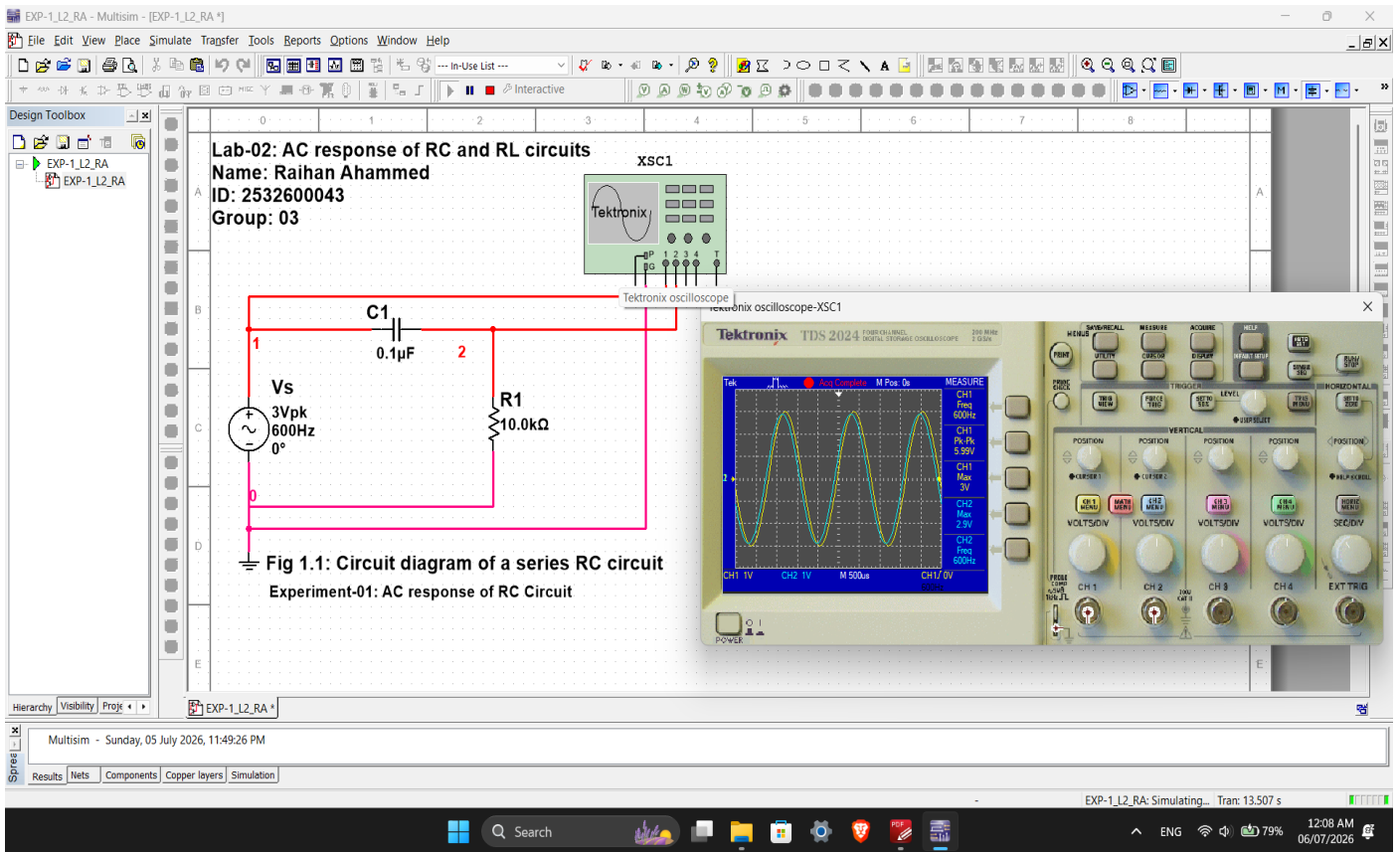
Name: Raihan Ahammed ID: 2532600043 Group: 03





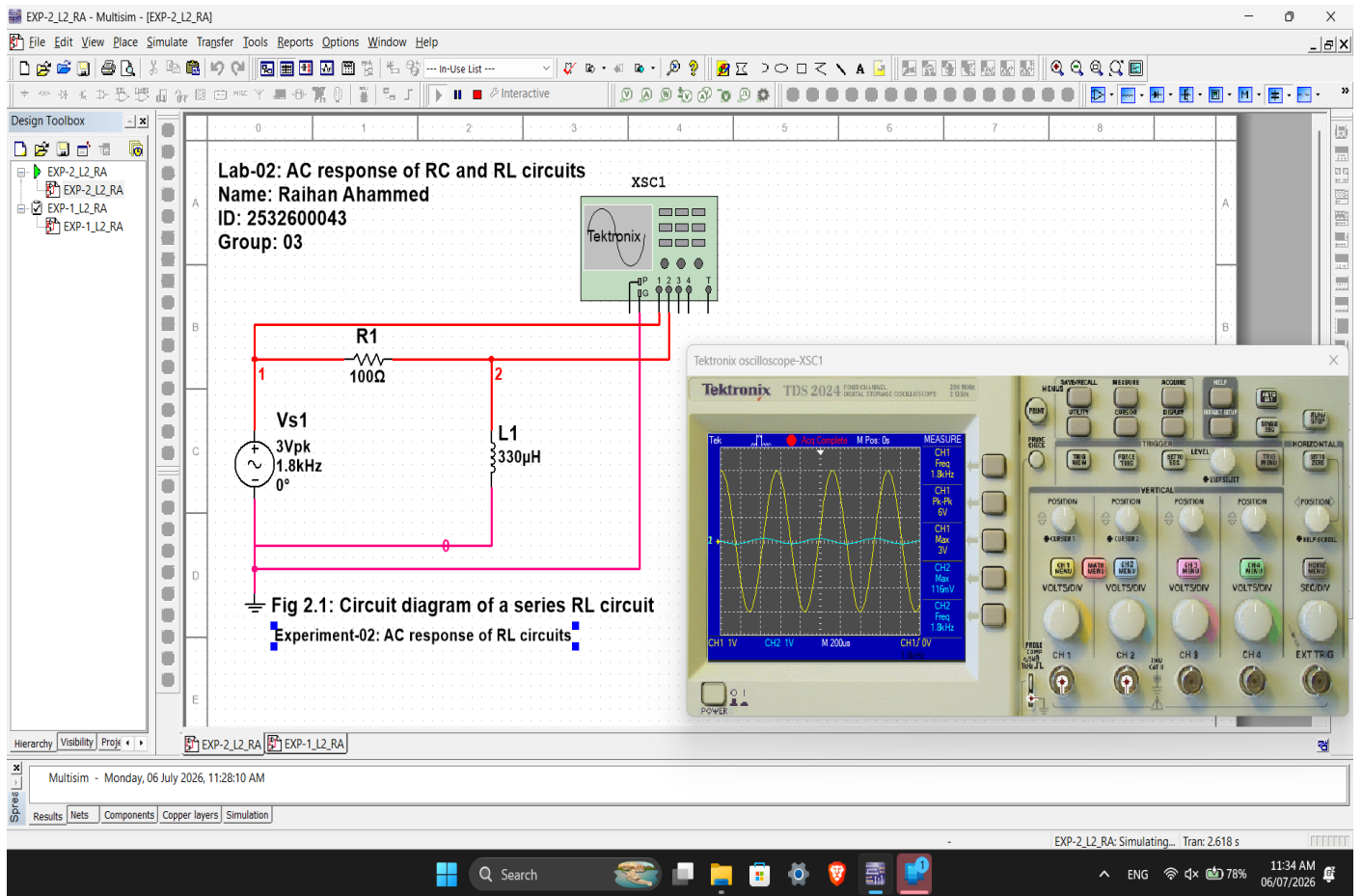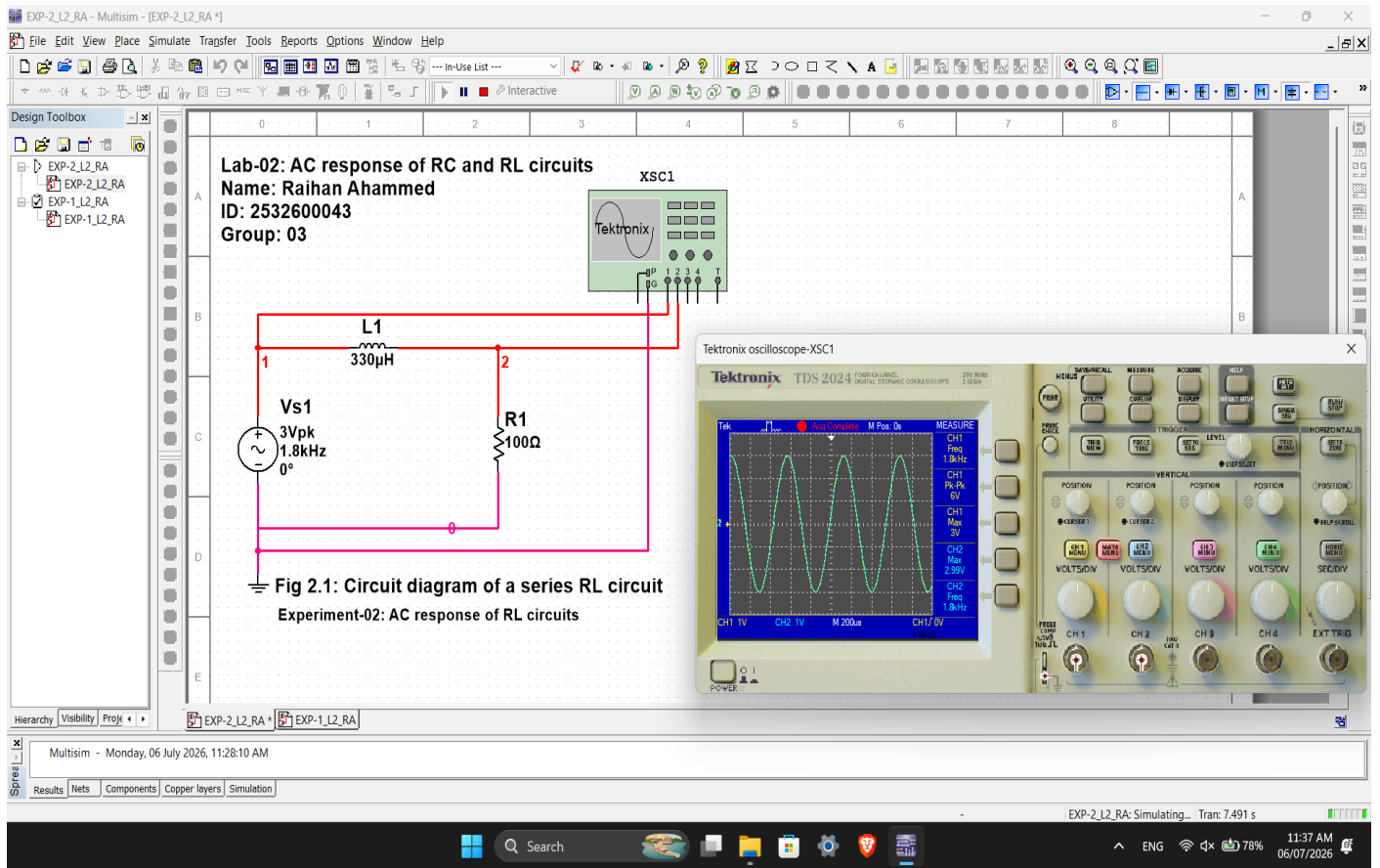



Lab-01: Verification of KVL and KCL

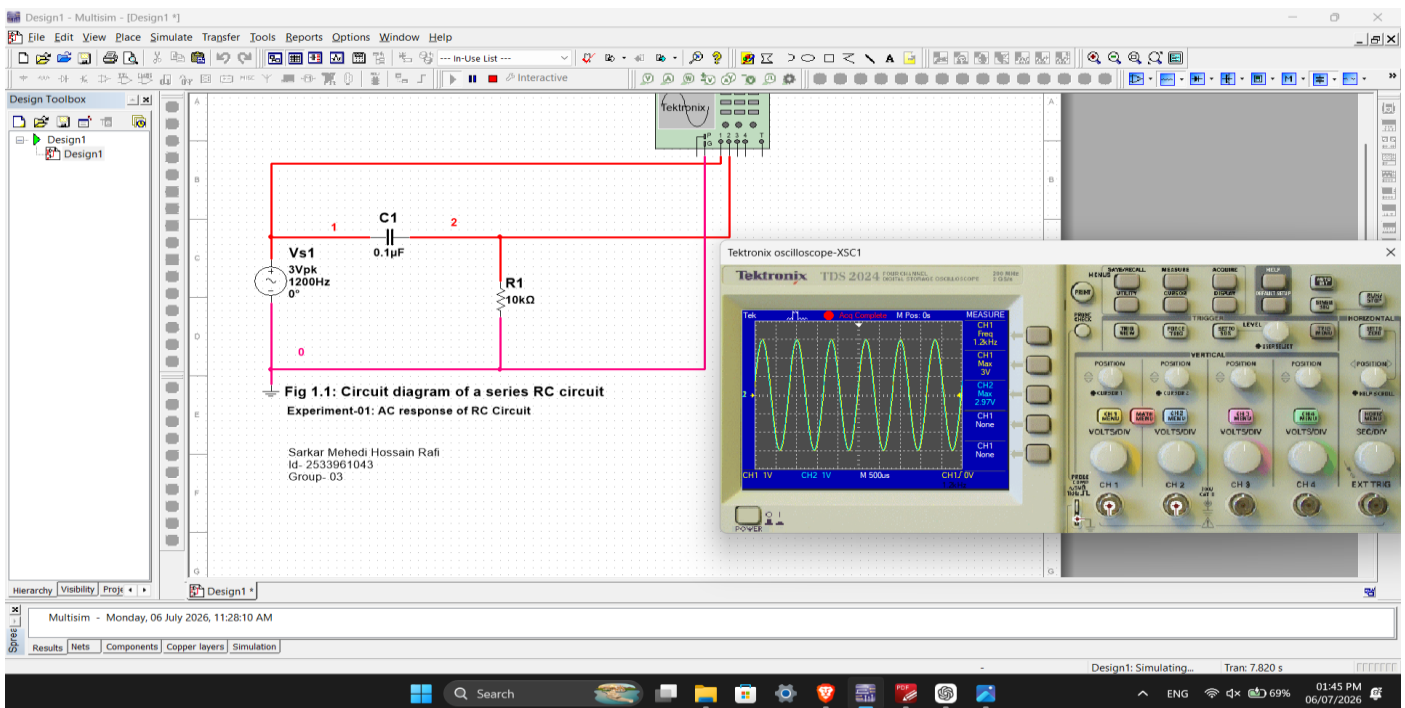
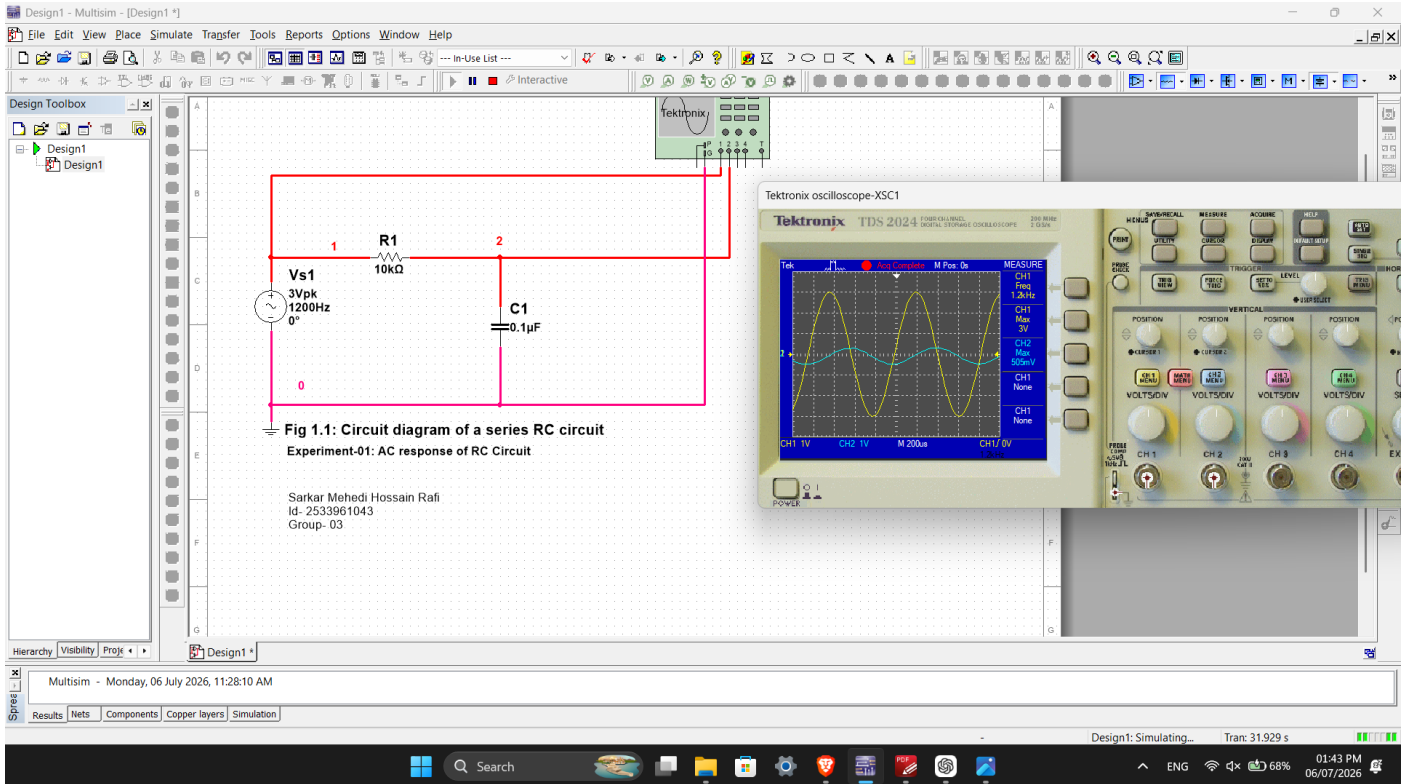
Name: Sarkar Mehedi Hossain Rafi ID: 2533961043 Group: 03



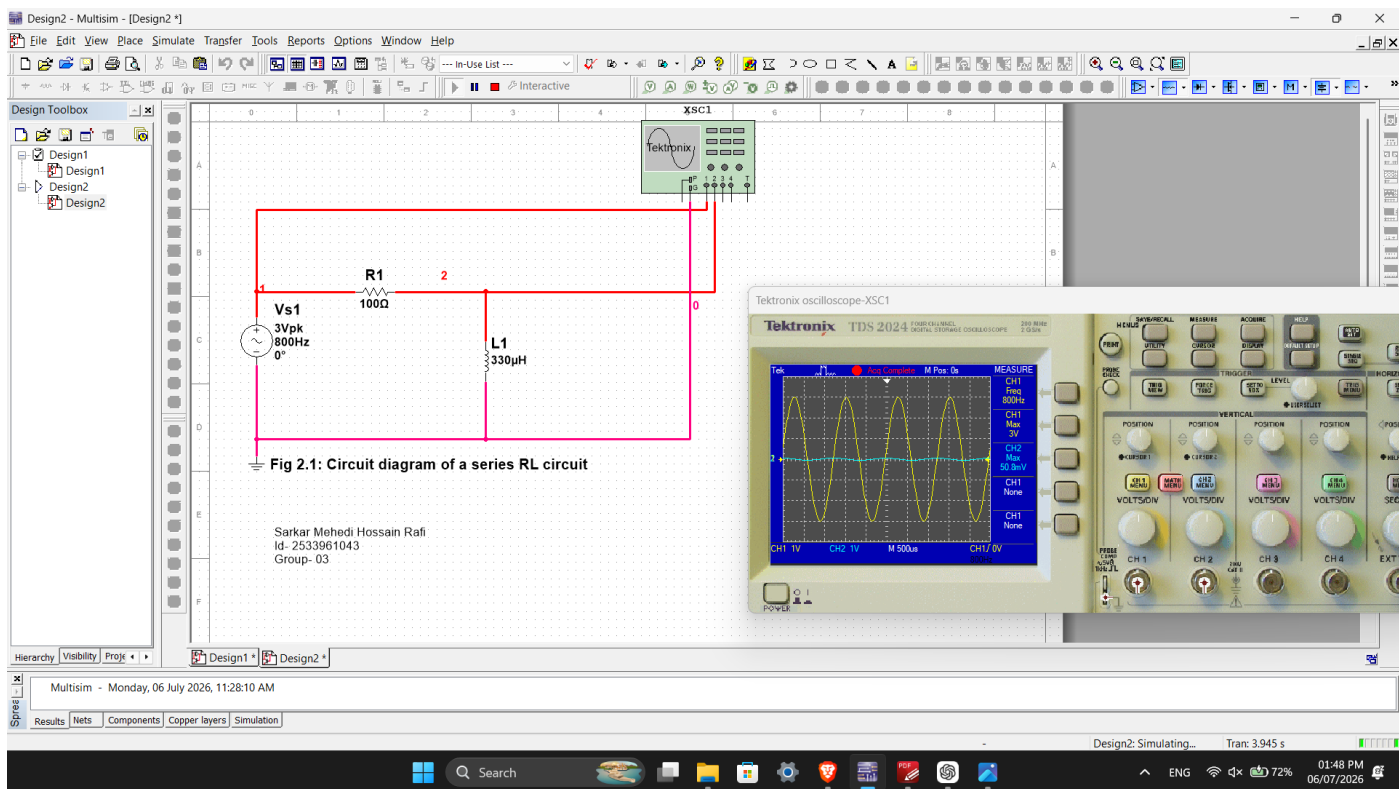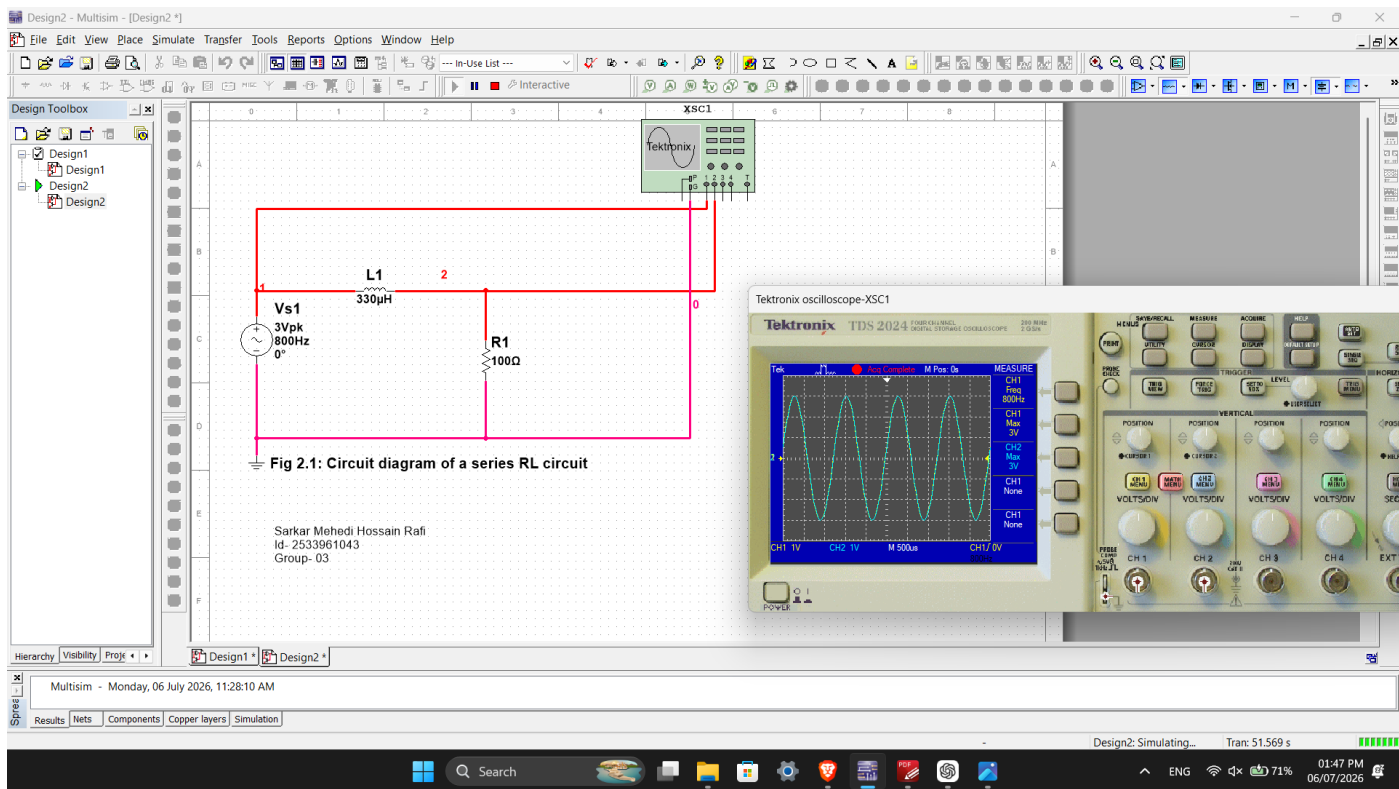


Name: ID: 2533961043 Group: 03

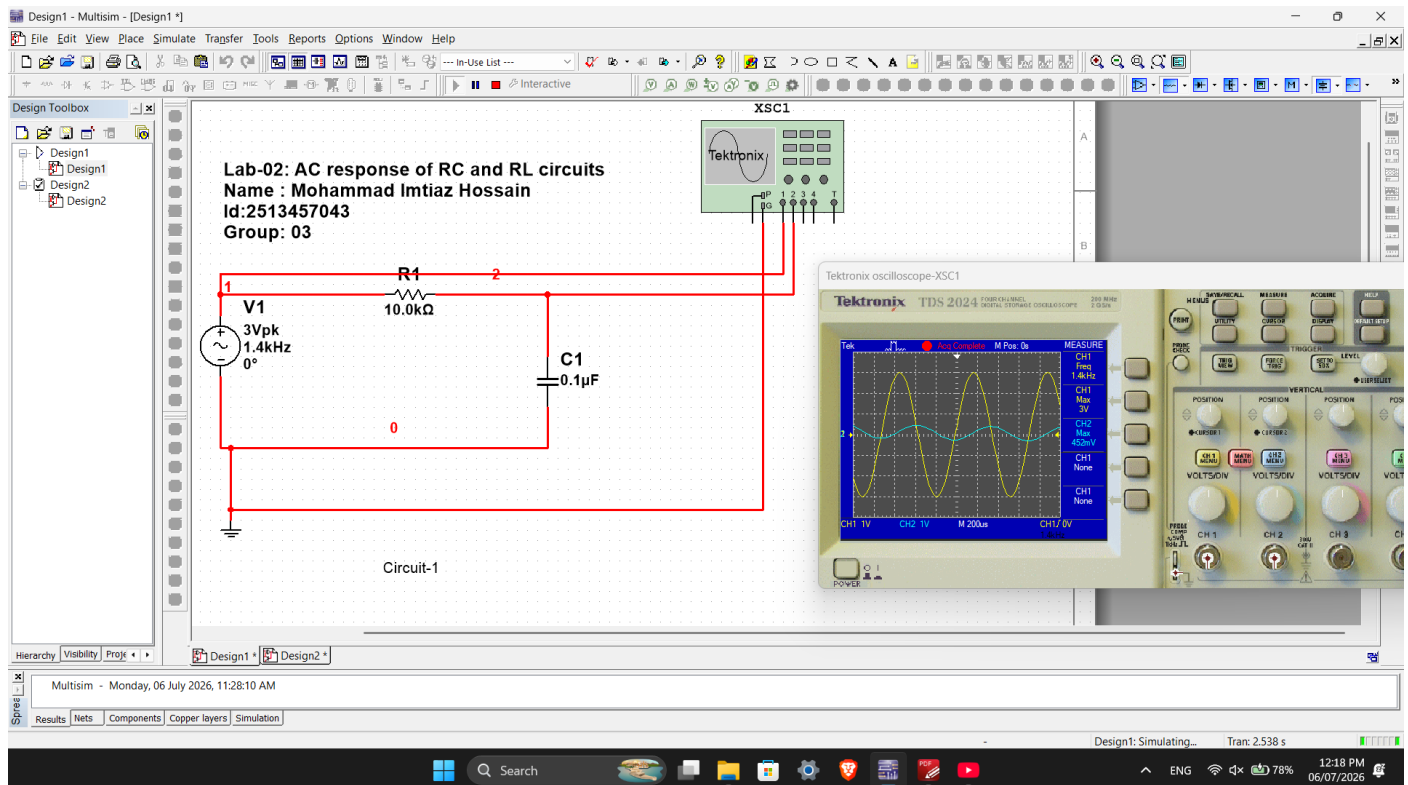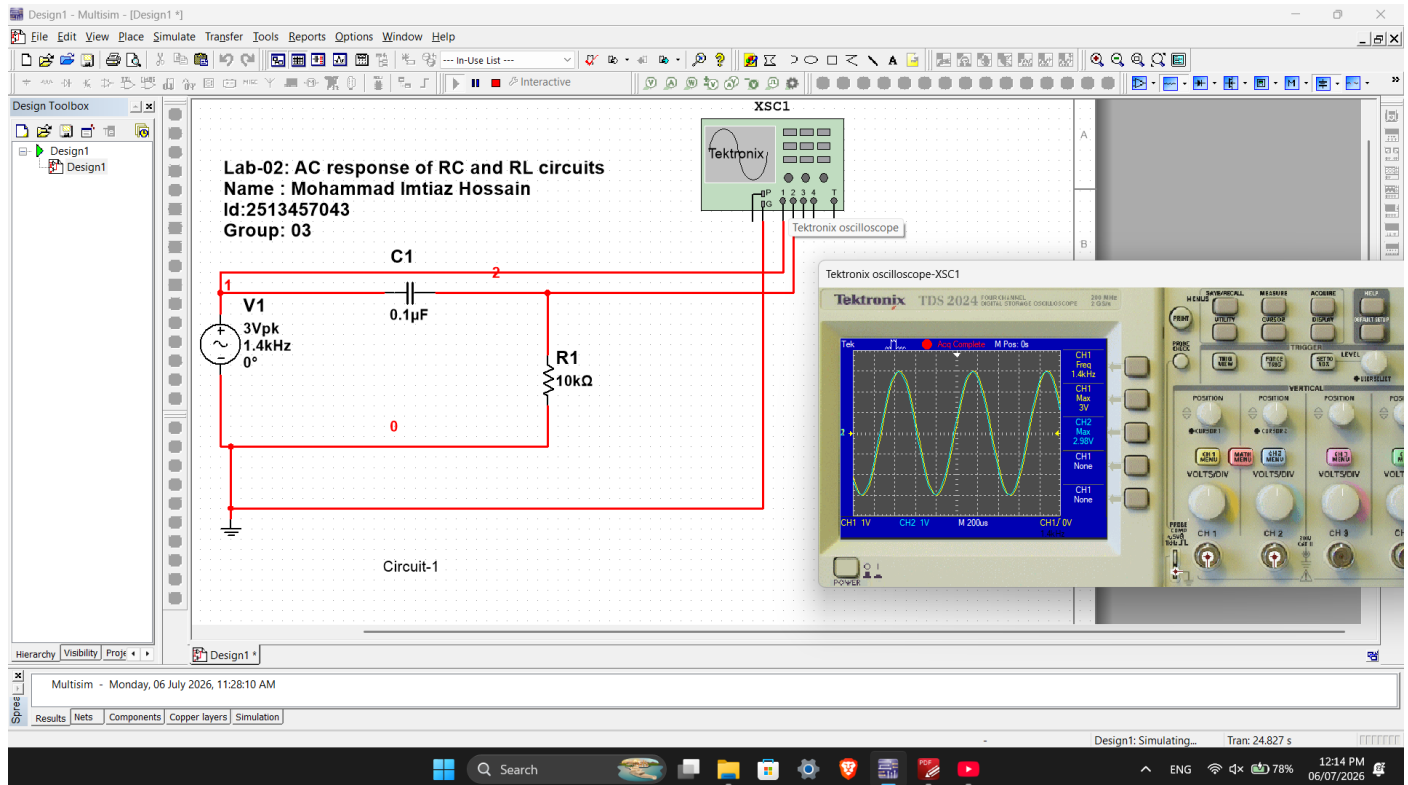


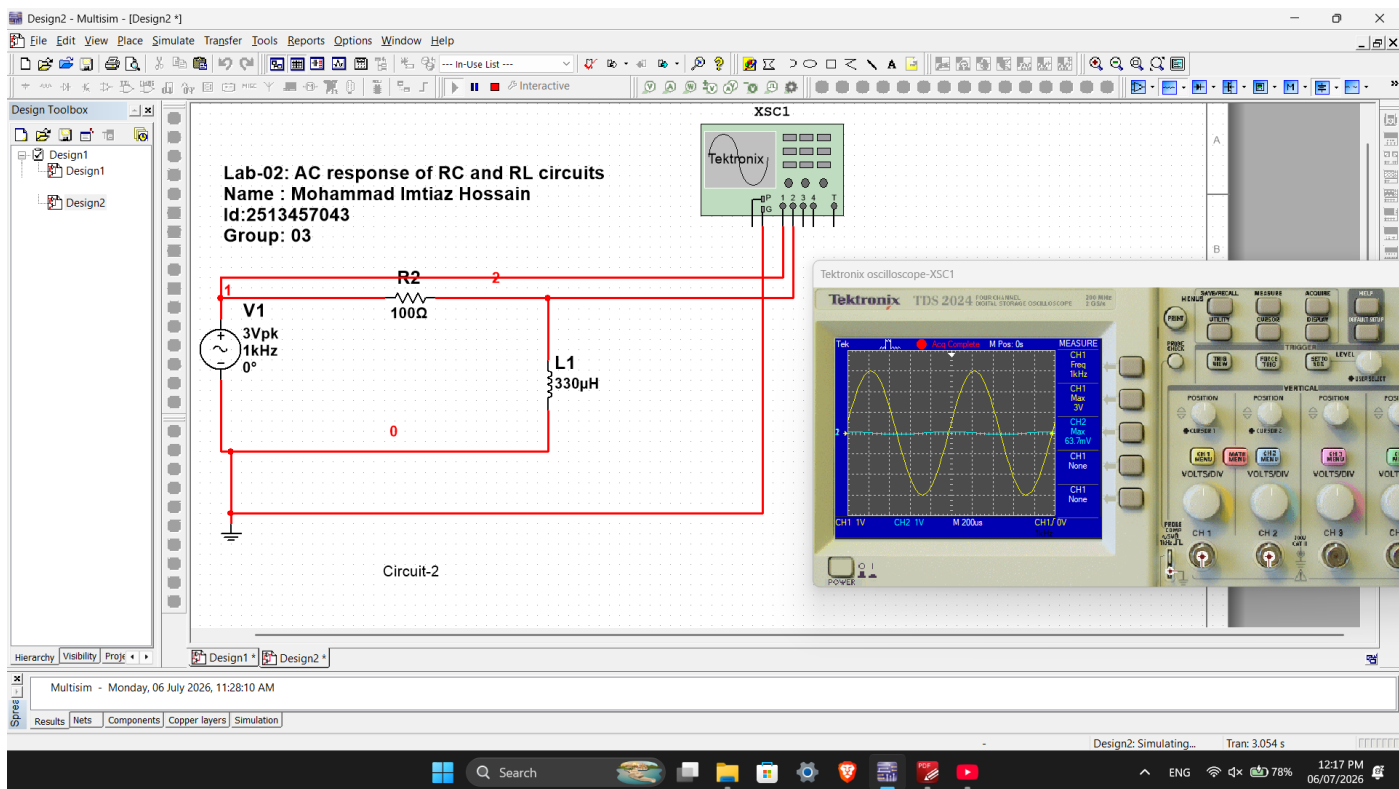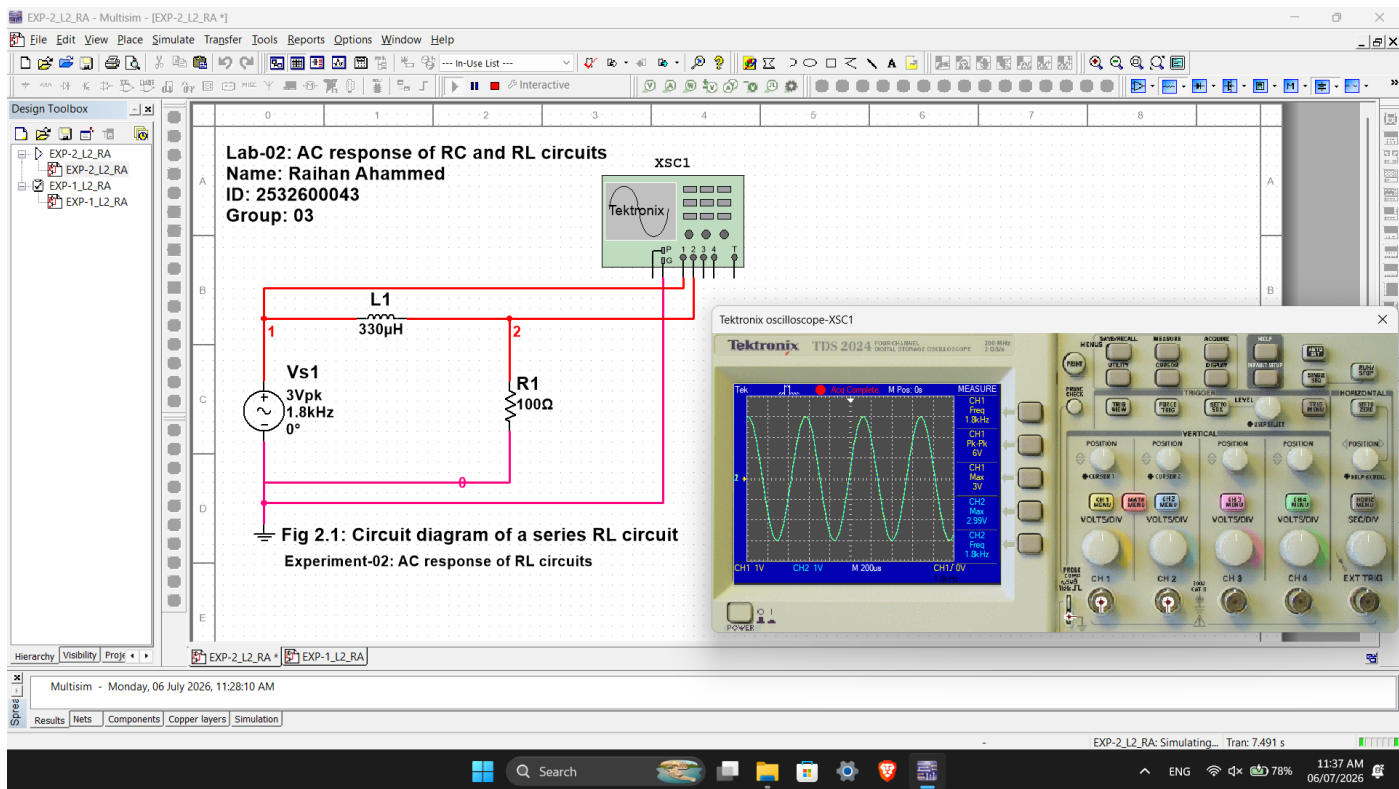


1. AC Response of C=0.1uF

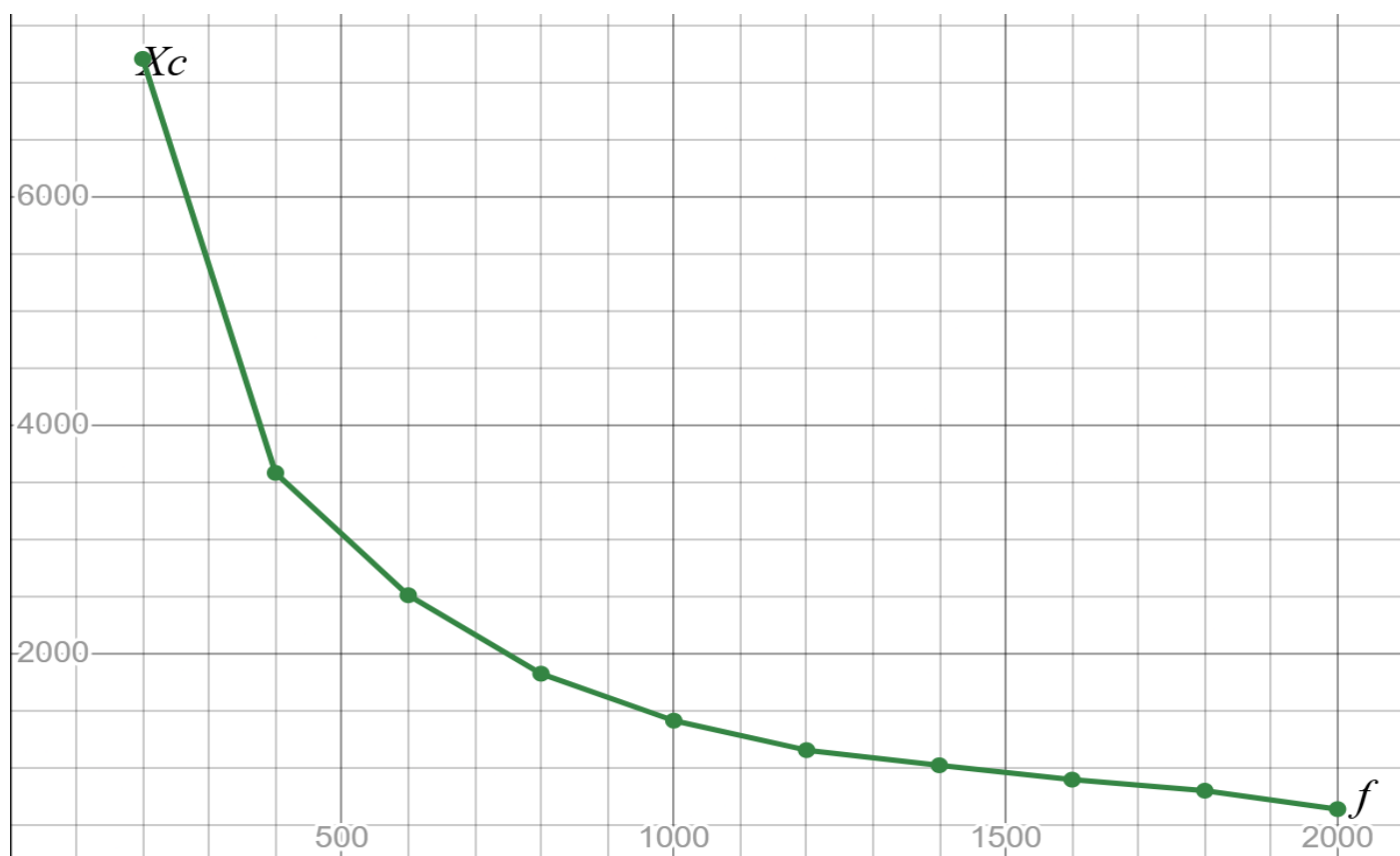

2. AC Response of C=0.4uF

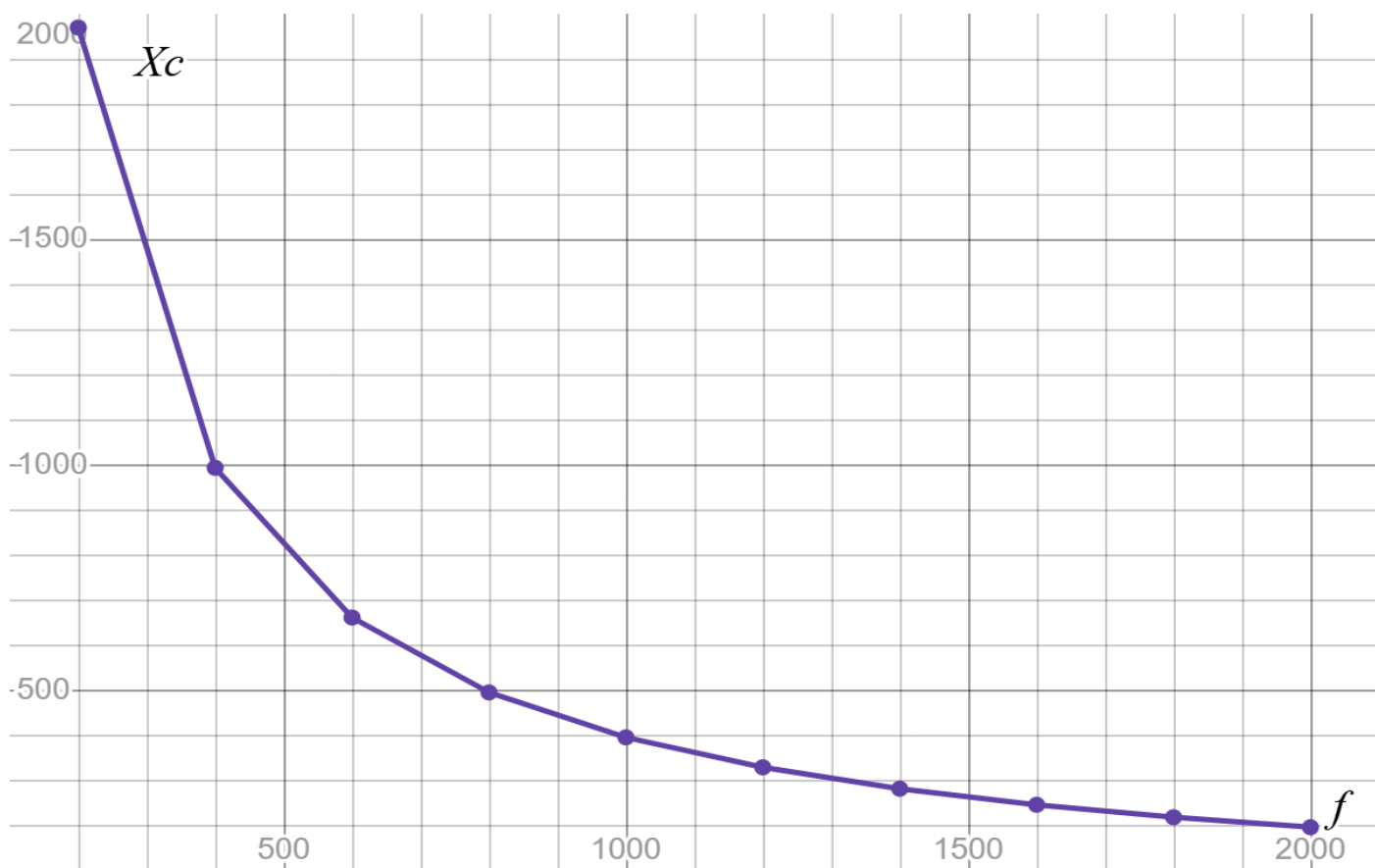

1. AC Response of L=330uH

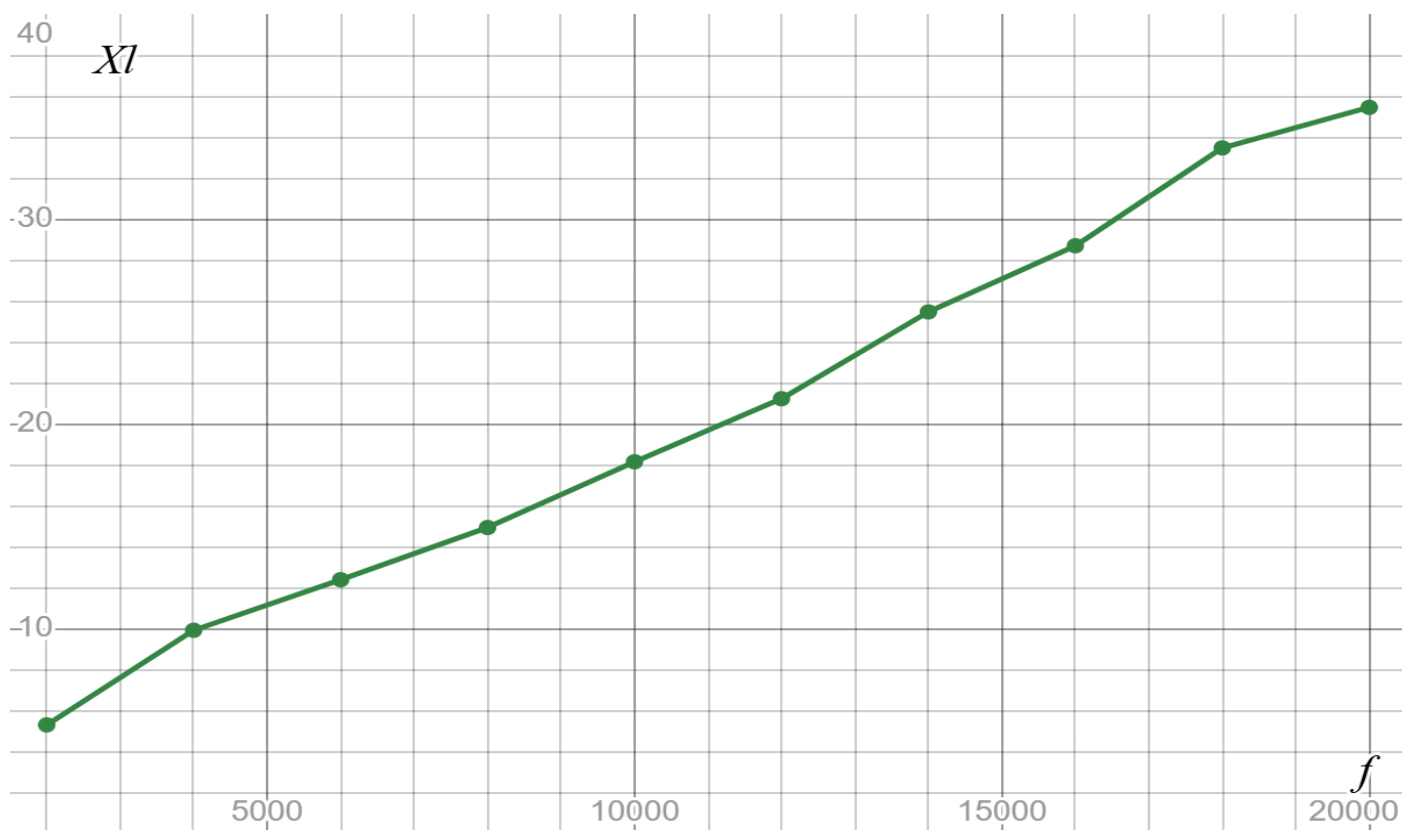

2. AC Response of L=600uH

